

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--

**T 3214**

B.E./B.Tech. DEGREE EXAMINATION, APRIL/MAY 2008.

Fourth Semester

(Regulation 2004)

Electronics and Communication Engineering

EC 1254 — LINEAR INTEGRATED CIRCUITS

(Common to B.E. (Part-Time) Third Semester Regulation 2005)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Define unity gain bandwidth of an OP-Amp.
2. Define slew rate. What causes it?
3. Draw the circuit diagram of a non-inverting amplifier.
4. Give any four applications of a comparator.
5. What is FSK technique?
6. Draw the circuit of AM detector using PLL.
7. Which type ADC is the fastest? Why?
8. What is adaptive delta modulation?
9. What is a switched capacitor filter?
10. List the characteristics of optocoupler.

PART B — (5 × 16 = 80 marks)

11. (a) What is a current mirror? Discuss in detail the Wildar current source. (16)

Or

- (b) Explain :
- (i) Band gap reference. (12)
  - (ii) Methods of improving slew rate. (4)

12. (a) (i) Explain the operation of Instrumentation amplifier. (8)
- (ii) Detail the working of Log and Antilog amplifiers. (8)

Or

- (b) With a neat circuit, explain the operation of Schmitt trigger. (16)

13. (a) (i) Explain PLL used as an Am Detection. (8)
- (ii) Explain how frequency multiplication is done using PLL. (8)

Or

- (b) (i) With a neat sketch, explain the working of variable transconductance multiplier. (10)
- (ii) Write notes on frequency synthesiser. (6)

14. (a) (i) Explain the working of Dual scope ADC. (8)
- (ii) With a neat circuit, explain the operation of a Binary weighted resistor D/A converter. (8)

Or

- (b) (i) Write notes on Analog switches. (6)
- (ii) Explain Delta modulation. What are its advantages and disadvantages? (10)

15. (a) What are the various blocks that form a Basic Voltage Regulator? Explain the series and shunt voltage regulator. List advantages of IC voltage regulators. (16)

Or

- (b) (i) Discuss the operation of IC 555 as a monostable multivibrator. Draw the waveform and explain. (8)
- (ii) Draw the functional block diagram of switching regulator and explain. (8)
- 

[www.collegebudies.blogspot.com](http://www.collegebudies.blogspot.com) → Administrator Mr. **VARUNA.V** B.E